

Chapter 4

Boolean Algebra and Logic Simplification (布尔代数和逻辑简化)

4-1 BOOLEAN OPERATIONS AND EXPRESSIONS

(布尔运算和表达式)

- Boolean algebra is the mathematics of digital systems.
(布尔代数是数字系统的数学工具)
- A variable is a symbol (usually an italic uppercase letter) used to represent a logic quantity. Any single variable can have a 1 or 0 value.
(通常用一个斜体大写字母表示一个变量。一个单变量的取值为0或者1)

4-1 BOOLEAN OPERATIONS AND EXPRESSIONS

(布尔运算和表达式)


- The **complement** is the inverse of a variable and is indicated by a bar over the variable (overbar). The complement of the variable A is read as "not A " or " A bar". Sometimes a prime symbol rather than an overbar is used to denote the complement of a variable.
- 一个变量的反码也称之为补码，通常用符号上面的一横表示。读作“not A ” or “ A bar”。有时候也用一撇代替一横杠，用来表示一个变量的反码/补码

A	$\overline{A}$	A'
$A + B,$	$A + B + \overline{C},$	$\overline{A} + B + C + \overline{D}$
$AB,$	$ABC\overline{C},$	$\overline{A}BC\overline{D}$


- Literal (因子) : Variable or complement of a variable

Boolean Operations and Expressions

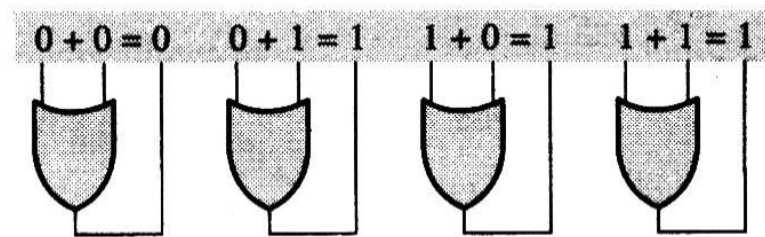- Boolean addition is equivalent to the OR operation and the basic rules are illustrated with their relation to the OR gates as follows:



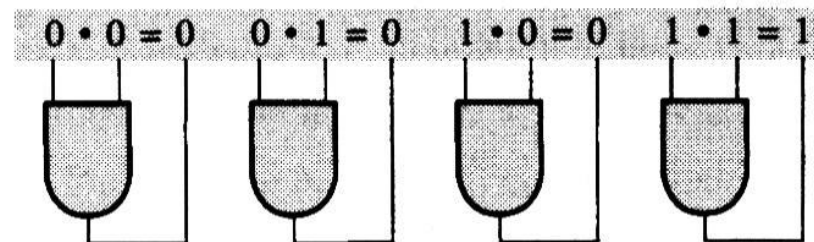- Boolean multiplication is equivalent to the AND operation and the basic rules are illustrated with their relation to the AND gates as follows:



AND (Boolean Multiplication) : $\cdot$

e.g. $A \text{ AND } B = A \cdot B = AB$

OR (Boolean Addition): $+$

e.g. $A \text{ OR } B = A+B$

Inverter(NOT): $\bar{}$

e.g. $\bar{A}$

sum term (求和项)

sum term: sum of literals. (Literal (因子) :
Variable or complement of a variable)

e.g. $A + B, A + \bar{B} + \bar{C}, \bar{A} + B + \bar{C} + D$

Example:

Determine the value of A, B, C , and D which
make the sum term $A + \bar{B} + C + \bar{D} = 0$

Solution:

$$A + \bar{B} + C + \bar{D} = 0 \longrightarrow A = 0, \bar{B} = 0, C = 0, \bar{D} = 0$$

$$\longrightarrow A = 0, B = 1, C = 0, D = 1$$

product term (乘积项)

product term: product of literals.

e.g. AB , $A\bar{B}C$, $A\bar{B}CD$

Example:

Determine the value of A , B , C , and D which make the product term $A\bar{B}C\bar{D} = 1$

Solution:

$$\begin{aligned} A\bar{B}C\bar{D} = 1 & \quad \longrightarrow \quad A = 1, \bar{B} = 1, C = 1, \bar{D} = 1 \\ & \quad \longrightarrow \quad A = 1, B = 0, C = 1, D = 0 \end{aligned}$$

4-2 LAWS AND RULES OF BOOLEAN ALGEBRA

布尔代数的定律和法则

	Laws	Boolean Expression
1	Commutative law of addition Commutative law of multiplication (交换律)	$A + B = B + A$ $AB = BA$
2	Associative law of addition Associative law of multiplication (结合律)	$A + (B + C) = (A + B) + C$ $A(BC) = (AB)C$
3	Distributive law (分配率)	$A(B + C) = AB + AC$

Laws and Rules of Boolean Algebra (I)

Rule Number	Boolean Expression
1	$A + 0 = A$
2	$A + 1 = 1$
3	$A \cdot 0 = 0$
4	$A \cdot 1 = A$
5	$A + A = A$
6	$A + \bar{A} = 1$

Laws and Rules of Boolean Algebra (II)

Rule Number	Boolean Expression
7	$A \cdot A = A$
8	$A \cdot \bar{A} = 0$
9	$\overline{\bar{A}} = A$
10	$A + AB = A$
11	$A + \bar{A}B = A + B$
12	$(A + B)(A + C) = A + BC$
13	$AB + \bar{A}C + BC = AB + \bar{A}C$

Laws and Rules of Boolean Algebra _PROOF (I)

- This law is similar to absorption in that it can be employed to **eliminate extra elements** from a Boolean expression:

$$A + \overline{A}B = A + B$$

[PROOF]

$$\begin{aligned} A + \overline{A}B &= A(1 + B) + \overline{A}B = (A + AB) + \overline{A}B \\ &= A + (AB + \overline{A}B) \\ &= A + (A + \overline{A})B \\ &= A + 1 \cdot B = A + B \end{aligned}$$

Laws and Rules of Boolean Algebra _PROOF (II)

$$(A + B)(A + C) = A + BC$$

[PROOF]

$$\begin{aligned}(A + B)(A + C) &= (A + B)A + (A + B)C \\&= AA + AB + AC + BC \\&= A + AB + AC + BC \\&= A(1 + B + C) + BC \\&= A + BC\end{aligned}$$

Laws and Rules of Boolean Algebra (III)

$$AB + \bar{A}C + BC = AB + \bar{A}C$$

[PROOF]

$$\begin{aligned} AB + \bar{A}C + BC &= AB + \bar{A}C + (A + \bar{A})BC \\ &= AB + \bar{A}C + ABC + \bar{A}BC \\ &= (AB + ABC) + (\bar{A}C + \bar{A}CB) = AB + \bar{A}C \end{aligned}$$

The key to using this theorem is to find a variable and its complement, note the associated terms, and eliminate the included term (the consensus term), which is composed of the associated terms.

4-3 DEMORGAN'S THEOREMS

狄摩根定理

- *DeMorgan's first theorem:*
- *The complement of a product of variables is equal to the sum of the complements of the variables.*

$$\overline{XY} = \bar{X} + \bar{Y}$$

(equivalency of the NAND and negative-OR gates)

Inputs		Output	
X	Y	$\overline{XY}$	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

- ***DeMorgan's second theorem:***

The complement of a sum of variables is equal to the product of the complements of the variables.

$$\overline{X + Y} = \overline{X} \overline{Y}$$

(equivalency of the NOR and negative-AND gates.)

Inputs		Output	
X	Y	$\overline{X + Y}$	$\overline{XY}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Apply DeMorgan's theorem to the expressions:

$$\overline{XYZ}, \overline{X + Y + Z}$$

Solution:

$$\begin{aligned}\overline{XYZ} &= \bar{X} + \overline{YZ} = \bar{X} + (\bar{Y} + \bar{Z}) \\ &= \bar{X} + \bar{Y} + \bar{Z}\end{aligned}$$

$$\overline{X + Y + Z} = \bar{X} \cdot \overline{Y + Z} = \bar{X}\bar{Y}\bar{Z}$$

Apply DeMorgan's theorems to each of the following expressions:

$$(a) \quad \overline{(A+B+C)D} \quad (b) \quad \overline{ABC+DEF}$$

Solution:

(a) Let $A+B+C=X$, $D=Y$:

$$\overline{(A+B+C)D} \longrightarrow \overline{XY} = \overline{X} + \overline{Y} = \overline{A+B+C} + \overline{D}$$

$$\overline{A+B+C} \longrightarrow \overline{A+B+C} = \overline{A}\overline{B}\overline{C}$$

$$\overline{(A+B+C)D} \longrightarrow \overline{A}\overline{B}\overline{C} + \overline{D}$$

$$\begin{aligned} (b) \quad \overline{ABC+DEF} &= \overline{(ABC)(DEF)} \\ &= (\overline{A} + \overline{B} + \overline{C})(\overline{D} + \overline{E} + \overline{F}) \end{aligned}$$

Example: Apply DeMorgan's theorem to the following expression:

$$\overline{\overline{A + B\overline{C}} + D(\overline{E + \overline{F}})}$$

Solution:

$$\overline{\overline{A + B\overline{C}} + D(\overline{E + \overline{F}})}$$

$$\overline{X + Y} = \overline{X}\overline{Y}$$

$$\Rightarrow = (\overline{A + B\overline{C}})(\overline{D(\overline{E + \overline{F}})})$$

$$\overline{XY} = \overline{X} + \overline{Y}$$

$$\Rightarrow = (A + B\overline{C})(\overline{D} + \overline{\overline{E + \overline{F}}})$$

$$\Rightarrow = (A + B\overline{C})(\overline{D} + E + \overline{F})$$

$$= A\overline{D} + AE + A\overline{F} + B\overline{C}\overline{D} + B\overline{C}E + B\overline{C}\overline{F}$$

4.4 Logic function Simplification (逻辑函数化简)

Objective:

To reduce a particular expression in its *simplest form* or *change its form to a more convenient one* to implement the expression most efficiently. The approach taken in this section is to use the *basic laws, rules, and theorems* of Boolean algebra to simplify an expression.

- Example 4-5 Using Boolean algebra, simplify this expression:

$$X = AB + A(B + C) + B(B + C)$$

- Solution:

$$X = AB + A(B + C) + B(B + C)$$


$$= AB + AB + AC + BB + BC$$

$$= AB + AB + AC + B + BC$$



$$= AB + AC + B + BC$$

$$= AB + AC + B$$

$$= AC + B$$

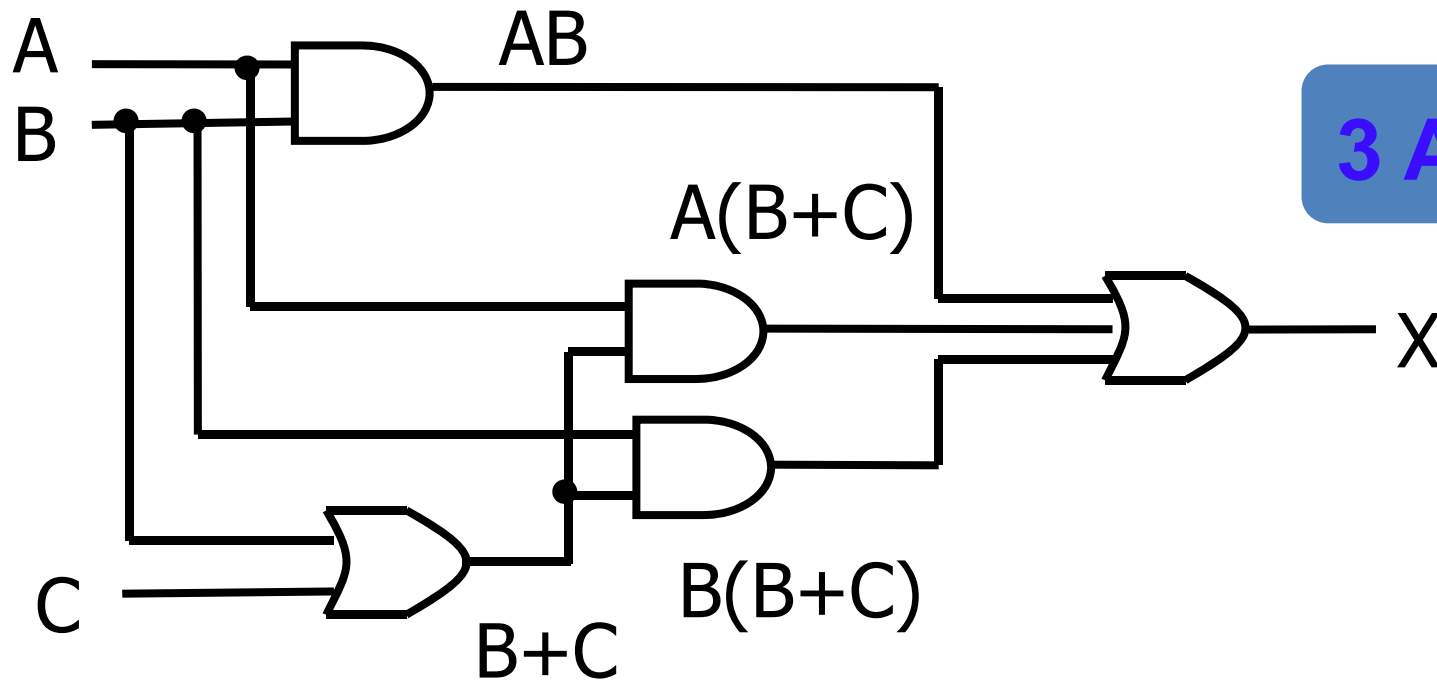

3 AND, 2 OR

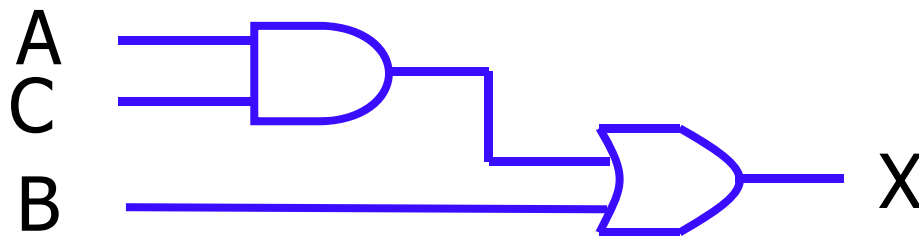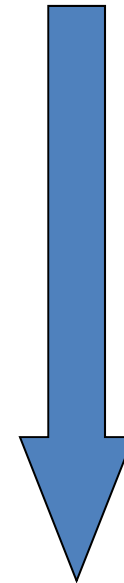

1 AND, 1 OR

Example:

$$(\overline{A}\overline{B}(C + BD) + \overline{A}\overline{B})C$$

Example:

$$(\overline{A}\overline{B}(C + BD) + \overline{A}\overline{B})C$$

$$= (\overline{A}\overline{B}C + \overline{A}\overline{B}BD + \overline{A}\overline{B})C$$

$$= (\overline{A}\overline{B}C + \overline{A} \cdot \underline{0} \cdot D + \overline{A}\overline{B})C$$

$$= (\overline{A}\overline{B}C + \overline{A}\overline{B})C$$

$$= \overline{A}\overline{B}CC + \overline{A}\overline{B}C$$

$$= \overline{A}\overline{B}C + \overline{A}\overline{B}C$$

$$= (\underline{A + \overline{A}})\overline{B}C$$

$$= 1 \cdot \overline{B}C$$

$$= \overline{B}C$$

4 AND, 2 OR



1 AND

Example

$$F = A\overline{B}CD + A\overline{B}CD = A$$

$$AB + A\overline{B} = A$$


$$2. A + AB = A$$

Example:

$$F = A + \overline{\overline{A} \cdot \overline{BC}} (\overline{A} + \overline{\overline{B} \overline{C}} + D) + BC$$

$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$

$$= A + BC + (A + BC)(\overline{A} + \overline{\overline{B} \overline{C}} + D)$$

$$A + AB = A$$

$$= A + BC$$

Example:

$$F = AC + \overline{A}D + \overline{C}D$$
$$= AC + (\overline{A} + \overline{C})D$$

$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$

$$= \textcircled{AC} + \textcircled{\overline{AC}D} \quad \leftarrow A + \overline{A}B = A + B$$

$$= AC + D$$

Example:

$$\begin{aligned} F &= \overline{A}B\overline{C} + \overline{A}BC + ABC \\ &= \overline{A}B\overline{C} + \underline{\overline{A}BC} + ABC \\ &= \overline{A}B\overline{C} + BC \\ &= B(\overline{A}\overline{C} + C) \\ &= B(\overline{A} + C) \\ &= \overline{A}B + BC \end{aligned}$$

Simplification Using Boolean Algebra

- Examples:

$$Y_1 = A\bar{B} + AC + BC$$

$$Y_2 = ABD + A\bar{B}\bar{C}\bar{D} + A\bar{C}DE + A$$

$$Y_3 = \bar{A}BC + (A + \bar{B})C$$

$$Y_4 = \overline{\overline{A}BC} + \overline{A\bar{B}}$$

$$Y_5 = A\bar{B}(\bar{A}CD + \overline{AD + \bar{B}\bar{C}})(\bar{A} + B)$$

$$Y_6 = AC(\bar{C}D + \bar{A}B) + BC\overline{\overline{\bar{B}} + AD + CE}$$

$$Y_7 = \overline{\overline{A}\bar{B}\bar{C}D + A\bar{C}DE + \bar{B}D\bar{E} + A\bar{C}\bar{D}E}$$