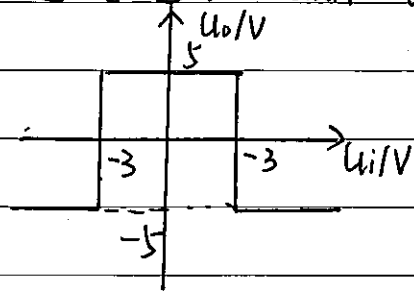


(e). $U_0 = \pm U_Z = \pm 5V$. $U_{RH} = U_T = 3V$, $U_{RL} = -3V$.



7.14. (a)

