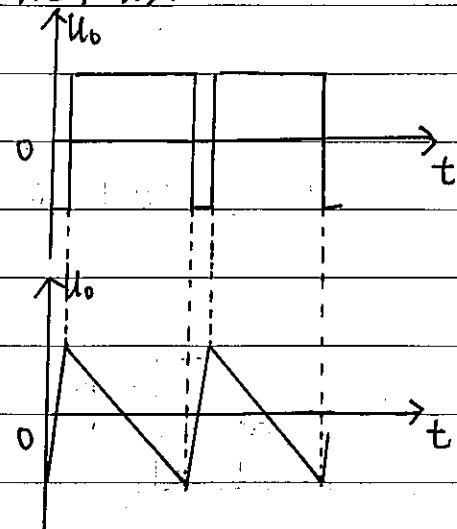


7.24 (1).



(2)  $U_T = \pm U_Z = \pm 8V$ .

$$\therefore -U_T = -\frac{1}{R_1 C} U_i T + U_T$$

$$\therefore T \approx \frac{2U_T R_1 C}{U_i}$$

$$\therefore f = \frac{U_i}{2U_T R_1 C} \approx 62.5 U_i$$