

7.2 (1) $\checkmark$ (2) $\times$ (3) $\checkmark$ (4) $\times$

7.6. (1) 由起振条件 $R_f + R'_w \geq 2R$:

$$\therefore R'_w \geq 2k\Omega.$$

$$(2) (f_0)_{\max} = \frac{1}{2\pi R_1 C} \approx 1.6kHz$$

$$(f_0)_{\min} = \frac{1}{2\pi C(R_1 + R_2)} \approx 145Hz.$$





7.7 (1). $\therefore R_f = 2R_1$.

$$\therefore U_o = U_f + U_1 = \frac{3}{2} U_z = \pm 9V$$



$$\text{有效值为 } U_o = \frac{9}{\sqrt{2}} V \approx 6.36V.$$

$$(2) f = \frac{1}{2\pi CR} \approx 9.95Hz.$$

7.9

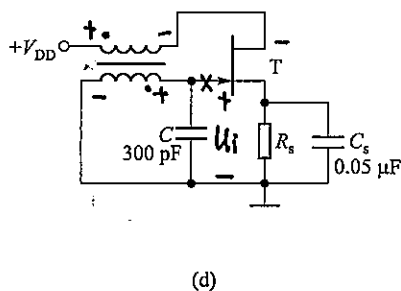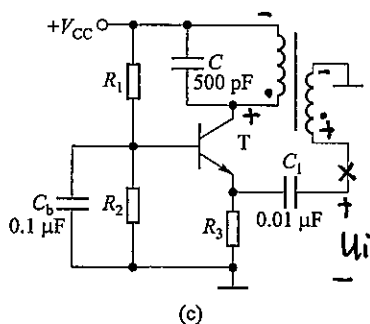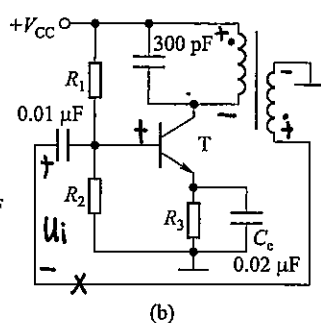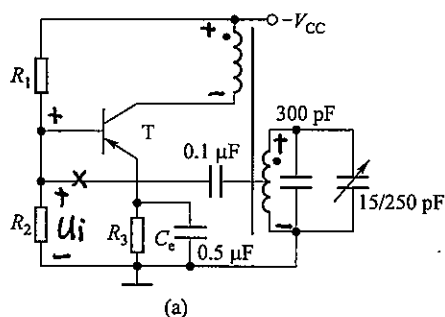

7.10. (a) 可能 (b) 不可能 (c) 不可能 (d) 可能.

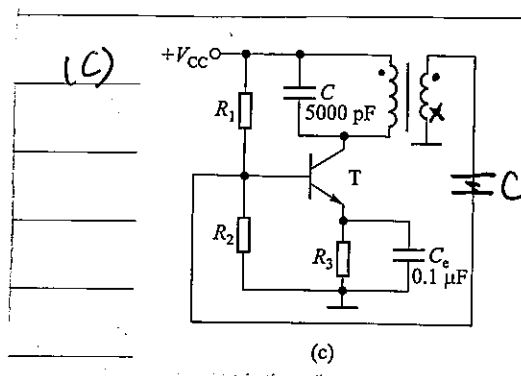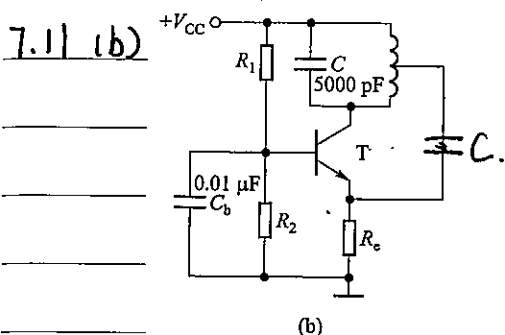

7.12(a) 选频网络: C 和 L .

正反馈网络: R_3 , C_2 和 R_W .

负反馈网络: C 和 L .

满足振荡条件


(b) 选频网络: C_2 和 L .

正反馈网络: R_4 , C_2 和 L .


负反馈网络: R_8 .

满足振荡条件.

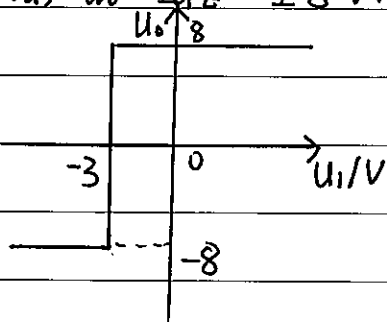7.13 (a) $U_o = \pm U_Z = \pm 8\text{V}$. $U_T = -\frac{R_1}{R_1} \cdot U_{REF} = -3\text{V}$.



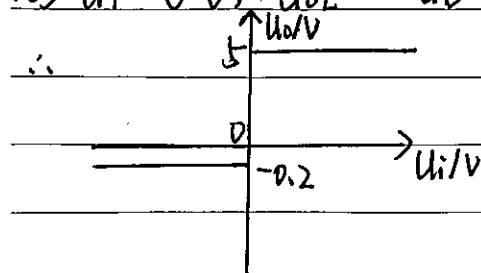(b) $U_T = 0 \text{ V}$, $U_{O1} = -U_D = -0.2 \text{ V}$, $U_{O1} = +U_Z = \pm 5 \text{ V}$.




(c). $U_O = \pm U_T = \pm 6 \text{ V}$.

$$U_p = \frac{R_1}{R_1 + R_2} U_O + \frac{R_2}{R_1 + R_2} U_{REF}$$

令 $U_p = U_n = U_1$, 则 $U_n = \frac{1}{3} U_O + 2$.

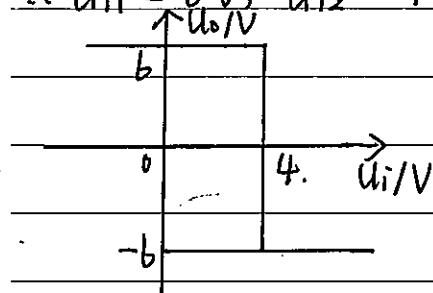$\therefore U_{T1} = 0 \text{ V}$, $U_{T2} = 4 \text{ V}$.




(d). $U_O = \pm U_Z = \pm 6 \text{ V}$.


$$U_p = \frac{R_2}{R_1 + R_2} U_1 + \frac{R_1}{R_1 + R_2} U_O = \frac{1}{3} U_O + \frac{2}{3} U_1$$

令 $U_p = U_n = 3 \text{ V}$, $U_1 = 9 = \frac{1}{2} (9 - U_O)$




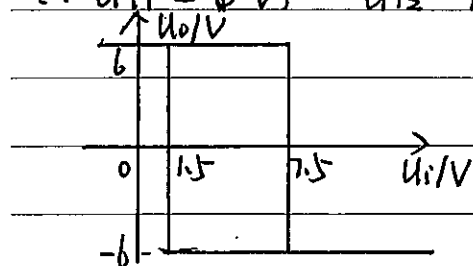
$\therefore U_{T1} = 1.5 \text{ V}$, $U_{T2} = 7.5 \text{ V}$.



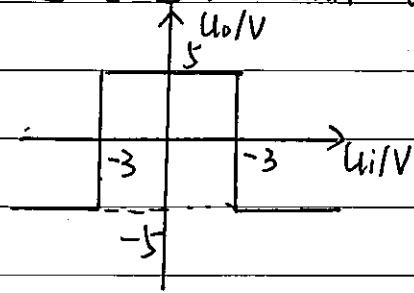(e). $U_0 = \pm U_Z = \pm 5V$. $U_{RH} = U_T = 3V$, $U_{RL} = -3V$.




7.14. (a)

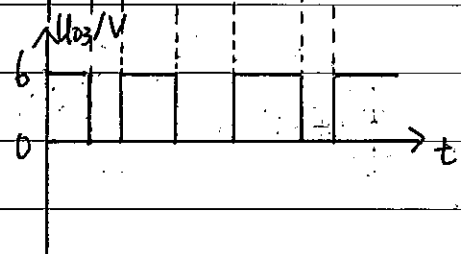
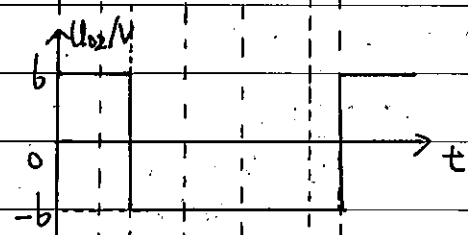
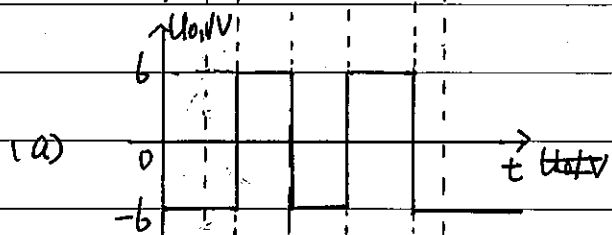
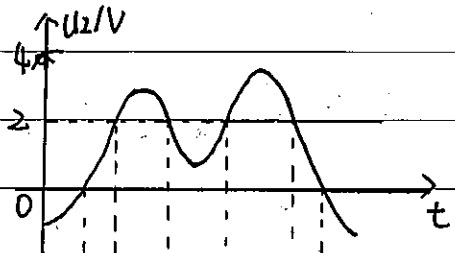


7.15 (b) 2端为“-”，3端为“+”，

反相输入的滞回比较器

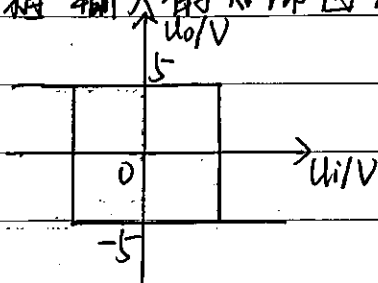

(c) ~~2~~ 2端为“-”，3端为“+”。

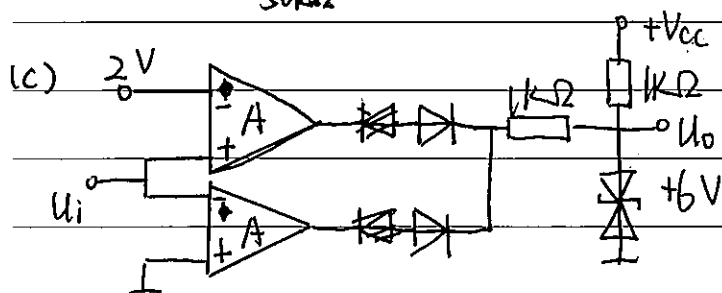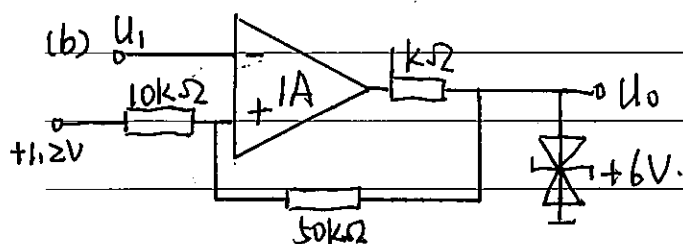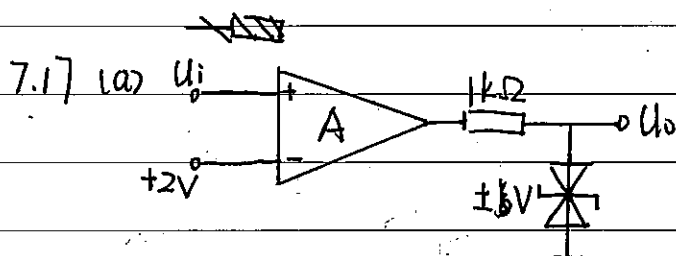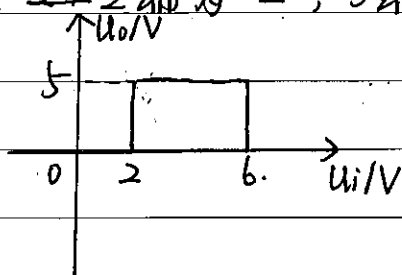

7.20. (2), (1), (3); (2), (1), (2); (1) (2) (2)

7.22

11) 温度信号 $\rightarrow$ 温度传感器 $\rightarrow$ 放大电路 $\rightarrow$ 压控振荡电路 $\rightarrow$ 频率计

12) 交流电压信号 $\rightarrow$ 放大电路 $\rightarrow$ 精密整流电路 $\rightarrow$ 低通滤波器 $\rightarrow$ 压控振荡电路 $\rightarrow$ 频率计

13) 文氏振荡桥 $\rightarrow$ C-ACV转换电路 $\rightarrow$ 精密整流电路 $\rightarrow$ 带通滤波器 $\rightarrow$ 压控振荡电路 $\rightarrow$ 频率计

7.23 (a) 当 $U_1 > 0$ 时, D_1, D_4 导通, D_2, D_3 截止, A_2 为电压跟随器, $U_0 = U_1$;

当 $U_1 < 0$ 时, D_2, D_3 导通, D_1, D_4 截止, A_1 为反相比例运算电路, 则 $U_0 = -\frac{R_4}{R_1} U_1 = -U_1$

$$\therefore U_0 = |U_1|$$

(b). 当 $U_1 > 0$ 时, D_1, D_4 导通, D_2, D_3 截止,


$$U_0 = \frac{R_4}{R_1} U_1$$

当 $U_1 < 0$ 时, D_1, D_4 截止, D_2, D_3 导通.

$$U_0 = -\frac{R_4}{R_1} U_1$$

$$\therefore U_0 = \frac{R_4}{R_1} |U_1|$$

7.24 (1).

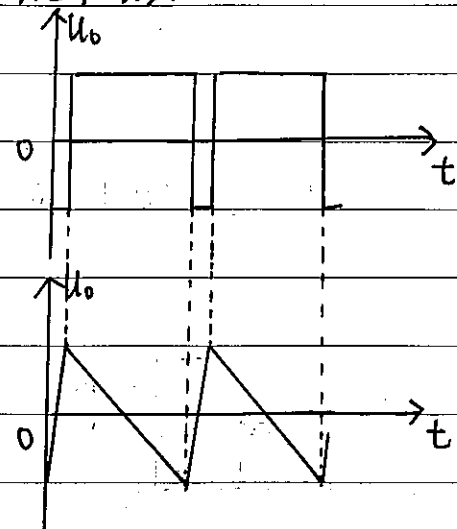

(2) $U_T = \pm U_Z = \pm 8V$.

$$\therefore -U_T = -\frac{1}{R_1 C} U_1 T + U_T$$

$$\therefore T \approx \frac{2U_T R_1 C}{U_1}$$

$$\therefore f = \frac{U_1}{2U_T R_1 C} \approx 62.5 U_1$$